

Problem 2 Circuit Measured in Lab 3-14-2018

C1 = 0.1105 uF

C2 = 0.1003 uF

 $R1 = 5030.5 \Omega$

 $R2 = 5022.1 \Omega$

 $R3(1) = 197.35 \Omega$

 $R3(2) = 197.55 \Omega$


 $R4 = 998.70 \Omega$


 $R5 = 996.20 \Omega$


+Vdd = +15.613 Vdc


-Vdd = -15.069 Vdc




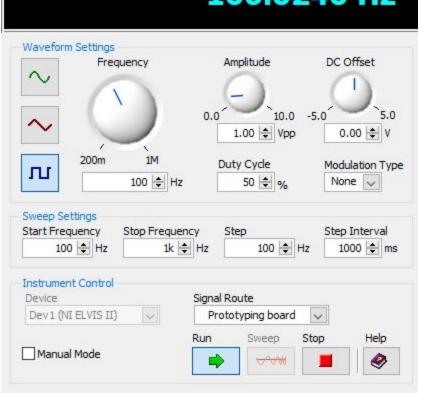

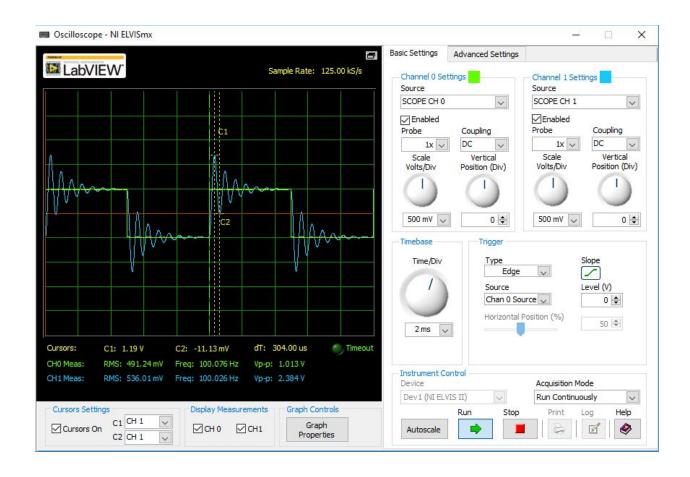

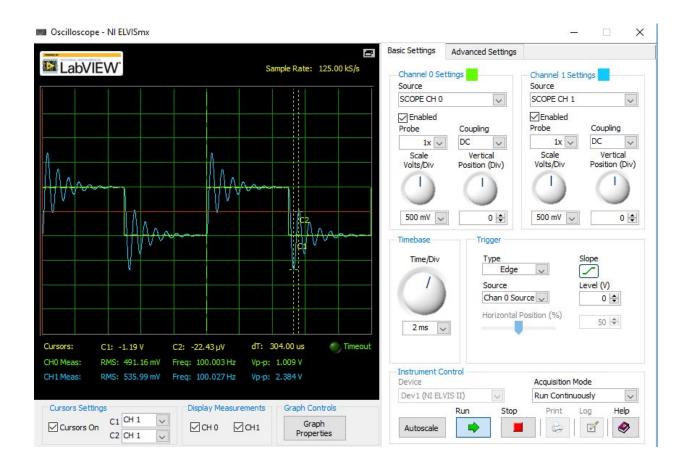

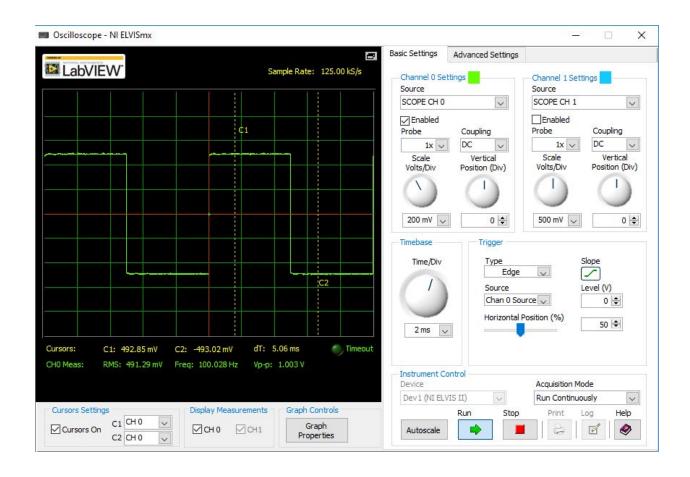

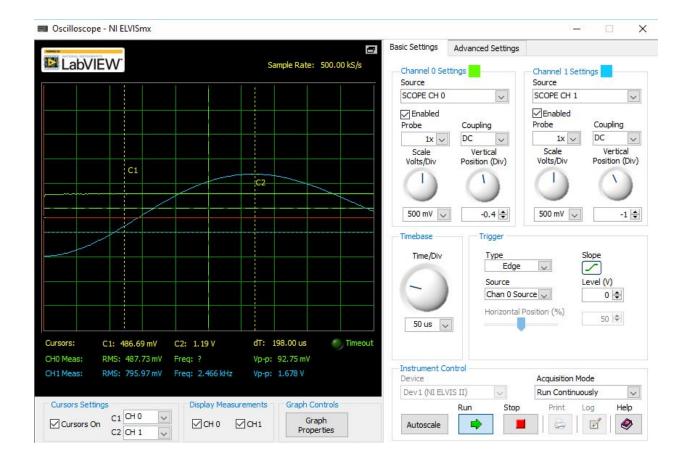

Problem 6 Circuit Measured in Lab 3-14-2018

C1 = 0.1105 uF

C2 = 0.1003 uF

 $R1 = 1283.2 \Omega$

 $R2 = 1292.7 \Omega$


 $R3 = 991.6 \Omega$


 $R4 = 998.70 \Omega$

 $R5 = 996.20 \Omega$

+Vdd = +15.613 Vdc

-Vdd = -15.069 Vdc

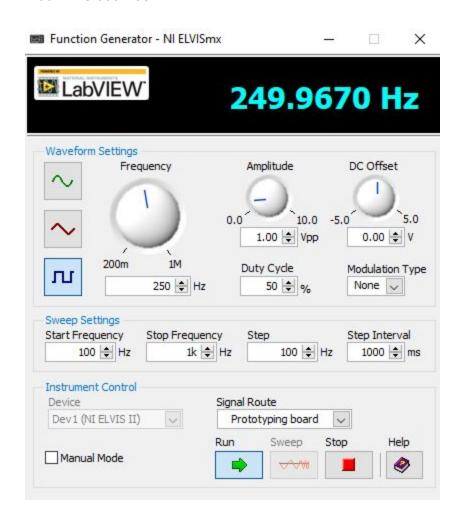

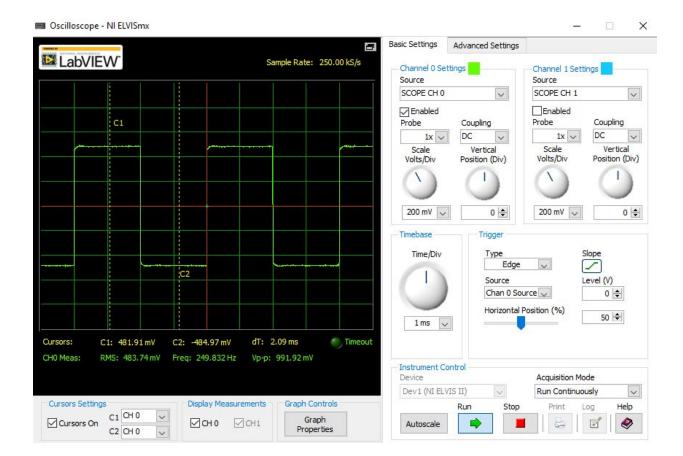

C2 CH 1

